

Міністерство освіти і науки України
Національний університет «Львівська політехніка»

Кафедра ЕОМ



Звіт

до лабораторної роботи № 3

з дисципліни «Моделювання комп'ютерних систем»
на тему:

«Поведінковий опис цифрового автомата Перевірка роботи автомата за
допомогою стенда Elbert V2 – Spartan 3A FPGA»

Варіант №10

Виконав:
ст. гр. КІ-201
Гришканич А. М.
Прийняв:
Козак Н. Б.

Львів 2024

Мета роботи: На базі стенда реалізувати цифровий автомат для обчислення значення виразів.

Виконання роботи:

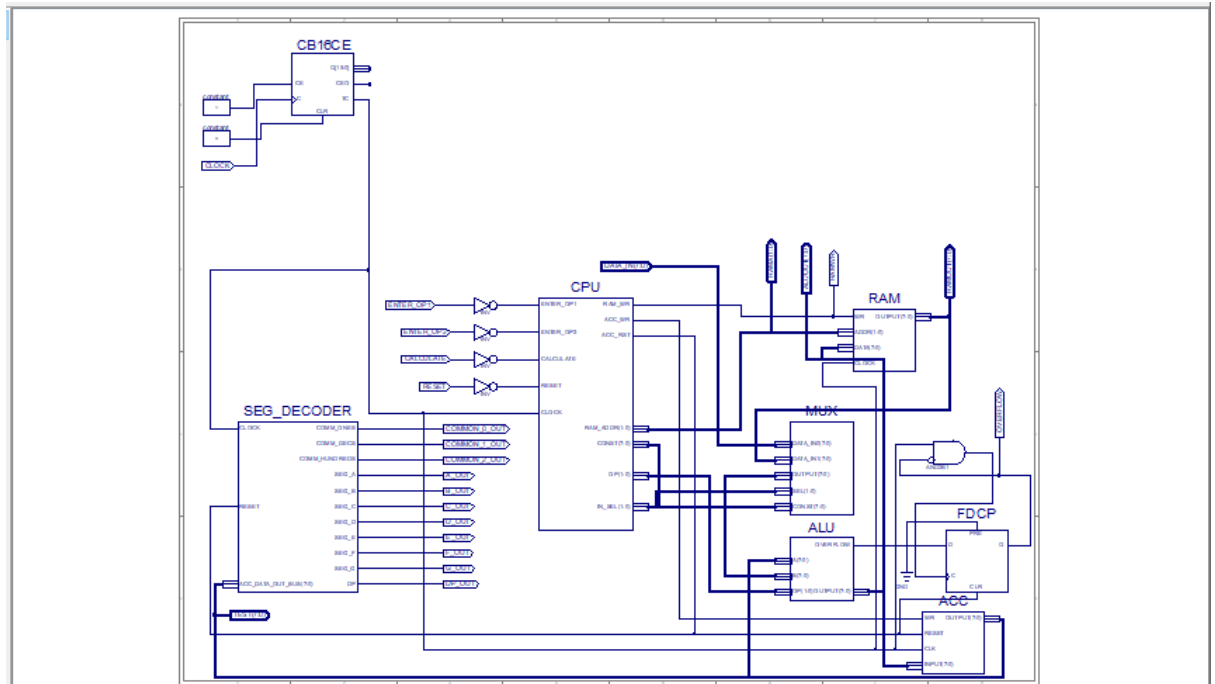


Рис. 1 – Top Level

Файл ACC.vhd

```

1. library IEEE;
2. use IEEE.STD_LOGIC_1164.ALL;
3.
4. -- Uncomment the following library declaration if using
5. -- arithmetic functions with Signed or Unsigned values
6. --use IEEE.NUMERIC_STD.ALL;
7.
8. -- Uncomment the following library declaration if instantiating
9. -- any Xilinx primitives in this code.
10. --library UNISIM;
11. --use UNISIM.VComponents.all;
12.
13. entity ACC is
14.     Port ( WR      : in  STD_LOGIC;
15.           RESET    : in  STD_LOGIC;
16.           CLK       : in  STD_LOGIC;
17.           INPUT     : in  STD_LOGIC_VECTOR (7 downto 0);
18.           OUTPUT    : out STD_LOGIC_VECTOR (7 downto 0));
19. end ACC;
20.
21. architecture ACC_arch of ACC is
22.     signal DATA : STD_LOGIC_VECTOR (7 downto 0);
23. begin
24.     process (CLK)
25.     begin
26.         if rising_edge(CLK) then
27.             if RESET = '1' then
28.                 DATA <= (others => '0');
29.             elsif WR = '1' then

```

```

30.          DATA <= INPUT;
31.      end if;
32.  end if;
33.  end process;
34.
35.
36.      OUTPUT <= DATA;
37.
38. end ACC_arch;
39.

```

Файл ALU.vhd

```

1. library IEEE;
2. use IEEE.STD_LOGIC_1164.ALL;
3.
4. -- Uncomment the following library declaration if using
5. -- arithmetic functions with Signed or Unsigned values
6. use IEEE.NUMERIC_STD.ALL;
7. use IEEE.STD_LOGIC_UNSIGNED.ALL;
8.
9. -- Uncomment the following library declaration if instantiating
10. -- any Xilinx primitives in this code.
11. --library UNISIM;
12. --use UNISIM.VComponents.all;
13.
14. entity ALU is
15.     Port ( A : in  STD_LOGIC_VECTOR(7 downto 0);
16.           B : in  STD_LOGIC_VECTOR(7 downto 0);
17.           OP : in  STD_LOGIC_VECTOR(1 downto 0);
18.           OUTPUT : out STD_LOGIC_VECTOR(7 downto 0);
19.           OVERFLOW: out STD_LOGIC);
20. end ALU;
21.
22.
23. architecture ALU_Behavioral of ALU is
24.     signal ALUR: STD_LOGIC_VECTOR(15 downto 0) := (others => '0');
25.     signal Carry: STD_LOGIC := '0';
26. begin
27.     process(A, B, OP)
28.     begin
29.         case (OP) is
30.             when "01" => ALUR <= ("00000000" & A) + ("00000000" & B);
31.             when "10" => ALUR <= ("00000000" & A) + ("11111111" & not
32. B) + "0000000000000001";
33.             when "11" =>
34.                 case(B) is
35.                     when x"00" => ALUR <=
36. std_logic_vector(unsigned(("00000000" & A)) sll 0);
37.                     when x"01" => ALUR <=
38. std_logic_vector(unsigned(("00000000" & A)) sll 1);
39.                     when x"02" => ALUR <=
40. std_logic_vector(unsigned(("00000000" & A)) sll 2);
41.                     when x"03" => ALUR <=
42. std_logic_vector(unsigned(("00000000" & A)) sll 3);
43.                     when x"04" => ALUR <=
44. std_logic_vector(unsigned(("00000000" & A)) sll 4);
45.                     when x"05" => ALUR <=
46. std_logic_vector(unsigned(("00000000" & A)) sll 5);
47.                     when x"06" => ALUR <=
48. std_logic_vector(unsigned(("00000000" & A)) sll 6);
49.                     when x"07" => ALUR <=
50. std_logic_vector(unsigned(("00000000" & A)) sll 7);
51.                     when others => ALUR <=
52. std_logic_vector(unsigned(("00000000" & A)) sll 0);

```

```

43.             end case;
44.             when others => ALUR <= ("00000000" & B);
45.         end case;
46.     end process;
47.     OUTPUT <= ALUR(7 downto 0);
48.     OVERFLOW <= ALUR(8) OR ALUR(9) OR ALUR(10) OR ALUR(11) OR ALUR(12) OR
        ALUR(13) OR ALUR(14) OR ALUR(15);
49. end ALU_Behavioral;

```

Файл CPU.vhd

```

1. library IEEE;
2. use IEEE.STD_LOGIC_1164.ALL;
3.
4.
5. entity CPU is
6.     port( ENTER_OP1 : IN STD_LOGIC;
7.           ENTER_OP2 : IN STD_LOGIC;
8.           CALCULATE : IN STD_LOGIC;
9.           RESET : IN STD_LOGIC;
10.          CLOCK : IN STD_LOGIC;
11.          RAM_WR : OUT STD_LOGIC;
12.          RAM_ADDR : OUT STD_LOGIC_VECTOR(1 DOWNTO 0);
13.          CONST : OUT STD_LOGIC_VECTOR(7 DOWNTO 0);
14.          ACC_WR : OUT STD_LOGIC;
15.          ACC_RST : OUT STD_LOGIC;
16.          IN_SEL : OUT STD_LOGIC_VECTOR(1 downto 0);
17.          OP : OUT STD_LOGIC_VECTOR(1 DOWNTO 0));
18. end CPU;
19.
20. architecture CPU_arch of CPU is
21.
22.     type STATE_TYPE is (RST, IDLE, LOAD_OP1, LOAD_OP2, RUN_CALC0, RUN_CALC1,
        RUN_CALC2, RUN_CALC3, RUN_CALC4, FINISH);
23.     signal CUR_STATE : STATE_TYPE;
24.     signal NEXT_STATE : STATE_TYPE;
25.
26.     begin
27.         SYNC_PROC: process (CLOCK)
28.         begin
29.             if (rising_edge(CLOCK)) then
30.                 if (RESET = '1') then
31.                     CUR_STATE <= RST;
32.                 else
33.                     CUR_STATE <= NEXT_STATE;
34.                 end if;
35.             end if;
36.         end process;
37.
38.
39.         NEXT_STATE_DECODE: process (CLOCK, ENTER_OP1, ENTER_OP2, CALCULATE)
40.         begin
41.             NEXT_STATE <= CUR_STATE;
42.
43.             case(CUR_STATE) is
44.                 when RST =>
45.                     NEXT_STATE <= IDLE;
46.                 when IDLE =>
47.                     if (ENTER_OP1 = '1') then
48.                         NEXT_STATE <= LOAD_OP1;
49.                     elsif (ENTER_OP2 = '1') then
50.                         NEXT_STATE <= LOAD_OP2;

```

```

51.             elsif (CALCULATE = '1') then
52.                 NEXT_STATE <= RUN_CALC0;
53.             else
54.                 NEXT_STATE <= IDLE;
55.             end if;
56.         when LOAD_OP1 =>
57.             NEXT_STATE <= IDLE;
58.         when LOAD_OP2 =>
59.             NEXT_STATE <= IDLE;
60.         when RUN_CALC0 =>
61.             NEXT_STATE <= RUN_CALC1;
62.         when RUN_CALC1 =>
63.             NEXT_STATE <= RUN_CALC2;
64.         when RUN_CALC2 =>
65.             NEXT_STATE <= RUN_CALC3;
66.         when RUN_CALC3 =>
67.             NEXT_STATE <= RUN_CALC4;
68.         when RUN_CALC4 =>
69.             NEXT_STATE <= FINISH;
70.         when FINISH =>
71.             NEXT_STATE <= FINISH;
72.         when others =>
73.             NEXT_STATE <= IDLE;
74.     end case;
75. end process;
76.
77.     OUTPUT_DECODE: process (CUR_STATE)
78.     begin
79.         case (CUR_STATE) is
80.             when RST =>
81.                 RAM_WR <= '0';
82.                 RAM_ADDR <= "00";
83.                 CONST <= "00000000";
84.                 ACC_WR <= '0';
85.                 ACC_RST <= '1';
86.                 IN_SEL <= "00";
87.                 OP <= "00";
88.             when LOAD_OP1 =>
89.                 RAM_WR <= '1';
90.                 RAM_ADDR <= "00";
91.                 CONST <= "00000000";
92.                 ACC_WR <= '0';
93.                 ACC_RST <= '1';
94.                 IN_SEL <= "00";
95.                 OP <= "00";
96.             when LOAD_OP2 =>
97.                 RAM_WR <= '1';
98.                 RAM_ADDR <= "01";
99.                 CONST <= "00000000";
100.                ACC_WR <= '0';
101.                ACC_RST <= '1';
102.                IN_SEL <= "00";
103.                OP <= "00";
104.             when RUN_CALC0 =>
105.                 RAM_WR <= '0';
106.                 RAM_ADDR <= "01";
107.                 CONST <= "00000000";
108.                 ACC_WR <= '1';
109.                 ACC_RST <= '0';
110.                 IN_SEL <= "01";
111.                 OP <= "00";
112.             when RUN_CALC1 =>
113.                 RAM_WR <= '0';
114.                 RAM_ADDR <= "00";
115.                 CONST <= "00000000";
116.                 ACC_WR <= '1';

```

```

117.             ACC_RST <= '0';
118.             IN_SEL <= "01";
119.             OP <= "10";
120.         when RUN_CALC2 =>
121.             RAM_WR <= '0';
122.             RAM_ADDR <= "00";
123.             CONST <= "00000001";
124.             ACC_WR <= '1';
125.             ACC_RST <= '0';
126.             IN_SEL <= "10";
127.             OP <= "11";
128.         when RUN_CALC3 =>
129.             RAM_WR <= '0';
130.             RAM_ADDR <= "00";
131.             CONST <= "00000000";
132.             ACC_WR <= '1';
133.             ACC_RST <= '0';
134.             IN_SEL <= "01";
135.             OP <= "01";
136.         when RUN_CALC4 =>
137.             RAM_WR <= '0';
138.             RAM_ADDR <= "00";
139.             CONST <= "00001010";
140.             ACC_WR <= '1';
141.             ACC_RST <= '0';
142.             IN_SEL <= "10";
143.             OP <= "01";
144.         when IDLE =>
145.             RAM_WR <= '0';
146.             RAM_ADDR <= "00";
147.             CONST <= "00000000";
148.             ACC_WR <= '0';
149.             ACC_RST <= '0';
150.             IN_SEL <= "00";
151.             OP <= "00";
152.         when others =>
153.             RAM_WR <= '0';
154.             RAM_ADDR <= "00";
155.             CONST <= "00000000";
156.             ACC_WR <= '0';
157.             ACC_RST <= '0';
158.             IN_SEL <= "00";
159.             OP <= "00";
160.         end case;
161.     end process;
162. end CPU_arch;

```

Файл MUX.vhd

```

1. library IEEE;
2. use IEEE.STD_LOGIC_1164.ALL;
3.
4. entity MUX is
5.     PORT(
6.         SEL: in STD_LOGIC_VECTOR(1 downto 0);
7.         CONST: in STD_LOGIC_VECTOR(7 downto 0);
8.         --CONST1: in STD_LOGIC_VECTOR()
9.         DATA_IN0: in STD_LOGIC_VECTOR(7 downto 0);
10.        DATA_IN1: in STD_LOGIC_VECTOR(7 downto 0);
11.        OUTPUT: out STD_LOGIC_VECTOR(7 downto 0)
12.    );
13. end MUX;
14.
15. architecture Behavioral of MUX is
16. begin

```

```

17.     process (SEL, DATA_IN0, DATA_IN1, CONST)
18.     begin
19.         if (SEL = "00") then
20.             OUTPUT <= DATA_IN0;
21.         elsif (SEL = "01") then
22.             OUTPUT <= DATA_IN1;
23.         else
24.             OUTPUT <= CONST;
25.         end if;
26.     end process;
27. end Behavioral;

```

Файл RAM.vhd

```

1. library IEEE;
2. use IEEE.STD_LOGIC_1164.ALL;
3. use IEEE.NUMERIC_STD.ALL;
4. use IEEE.STD_LOGIC_UNSIGNED.ALL;
5.
6.
7. entity RAM is
8.     port(
9.         WR : IN STD_LOGIC;
10.        ADDR : IN STD_LOGIC_VECTOR(1 DOWNTO 0);
11.        DATA : IN STD_LOGIC_VECTOR(7 DOWNTO 0);
12.        CLOCK: IN STD_LOGIC;
13.        OUTPUT : OUT STD_LOGIC_VECTOR(7 DOWNTO 0)
14.    );
15. end RAM;
16.
17. architecture RAM_arch of RAM is
18.     type ram_type is array (3 downto 0) of STD_LOGIC_VECTOR(7 downto 0);
19.     signal UNIT : ram_type;
20.
21. begin
22.     process(ADDR, CLOCK, UNIT)
23.     begin
24.         if(rising_edge(CLOCK)) then
25.             if (WR = '1') then
26.                 UNIT(conv_integer(ADDR)) <= DATA;
27.             end if;
28.         end if;
29.         OUTPUT <= UNIT(conv_integer(ADDR));
30.     end process;
31. end RAM_arch;

```

Файл SEG_DECODER.vhd

```

1. library IEEE;
2. use IEEE.STD_LOGIC_1164.ALL;
3. use IEEE.STD_LOGIC_ARITH.ALL;
4. use IEEE.STD_LOGIC_UNSIGNED.ALL;
5.
6.
7. entity SEG_DECODER is
8.     port( CLOCK : IN STD_LOGIC;
9.         RESET : IN STD_LOGIC;
10.        ACC_DATA_OUT_BUS : IN STD_LOGIC_VECTOR(7 DOWNTO 0);
11.        COMM_ONES      : OUT STD_LOGIC;

```

```

12.             COMM_DECS           : OUT STD_LOGIC;
13.             COMM_HUNDREDS      : OUT STD_LOGIC;
14.             SEG_A       : OUT STD_LOGIC;
15.             SEG_B       : OUT STD_LOGIC;
16.             SEG_C       : OUT STD_LOGIC;
17.             SEG_D       : OUT STD_LOGIC;
18.             SEG_E       : OUT STD_LOGIC;
19.             SEG_F       : OUT STD_LOGIC;
20.             SEG_G       : OUT STD_LOGIC;
21.             DP           : OUT STD_LOGIC);
22. end SEG_DECODER;
23.
24. architecture Behavioral of SEG_DECODER is
25.
26.     signal ONES_BUS : STD_LOGIC_VECTOR(3 downto 0) := "0000";
27.     signal DECS_BUS : STD_LOGIC_VECTOR(3 downto 0) := "0001";
28.     signal HONDREDS_BUS : STD_LOGIC_VECTOR(3 downto 0) := "0000";
29.
30. begin
31.     BIN_TO_BCD : process (ACC_DATA_OUT_BUS)
32.     variable hex_src : STD_LOGIC_VECTOR(7 downto 0) ;
33.     variable bcd      : STD_LOGIC_VECTOR(11 downto 0) ;
34.     begin
35.         bcd          := (others => '0') ;
36.         hex_src      := ACC_DATA_OUT_BUS;
37.
38.         for i in hex_src'range loop
39.             if bcd(3 downto 0) > "0100" then
40.                 bcd(3 downto 0) := bcd(3 downto 0) + "0011" ;
41.             end if ;
42.             if bcd(7 downto 4) > "0100" then
43.                 bcd(7 downto 4) := bcd(7 downto 4) + "0011" ;
44.             end if ;
45.             if bcd(11 downto 8) > "0100" then
46.                 bcd(11 downto 8) := bcd(11 downto 8) + "0011" ;
47.             end if ;
48.
49.             bcd := bcd(10 downto 0) & hex_src(hex_src'left) ; -- shift bcd + 1
50.             hex_src := hex_src(hex_src'left - 1 downto hex_src'right) & '0' ; --
51.             shift src + pad with 0
52.         end loop ;
53.
54.         HONDREDS_BUS      <= bcd (11 downto 8);
55.         DECS_BUS          <= bcd (7 downto 4);
56.         ONES_BUS          <= bcd (3 downto 0);
57.     end process BIN_TO_BCD;
58.
59.     INDICATE : process(CLOCK)
60.     type DIGIT_TYPE is (ONES, DECS, HUNDREDS);
61.
62.     variable CUR_DIGIT      : DIGIT_TYPE := ONES;
63.     variable DIGIT_VAL      : STD_LOGIC_VECTOR(3 downto 0) := "0000";
64.     variable DIGIT_CTRL     : STD_LOGIC_VECTOR(6 downto 0) :=
65.     "0000000";
66.     variable COMMONS_CTRL   : STD_LOGIC_VECTOR(2 downto 0) := "000";
67.
68.     begin
69.         if (rising_edge(CLOCK)) then
70.             if(RESET = '0') then
71.                 case CUR_DIGIT is
72.                     when ONES =>
73.                         DIGIT_VAL := ONES_BUS;
74.                         CUR_DIGIT := DECS;
75.                         COMMONS_CTRL := "001";

```



```

75.                                     when DECS =>
76.                                         DIGIT_VAL := DECS_BUS;
77.                                         CUR_DIGIT := HUNDREDS;
78.                                         COMMONS_CTRL := "010";
79.                                     when HUNDREDS =>
80.                                         DIGIT_VAL := HUNDREDS_BUS;
81.                                         CUR_DIGIT := ONES;
82.                                         COMMONS_CTRL := "100";
83.                                     when others =>
84.                                         DIGIT_VAL := ONES_BUS;
85.                                         CUR_DIGIT := ONES;
86.                                         COMMONS_CTRL := "000";
87.                                     end case;
88.
89.                                     case DIGIT_VAL is                                     --abcdefg
90.                                         when "0000" => DIGIT_CTRL :=
"1111110";
91.                                         when "0001" => DIGIT_CTRL :=
"0110000";
92.                                         when "0010" => DIGIT_CTRL :=
"1101101";
93.                                         when "0011" => DIGIT_CTRL :=
"1111001";
94.                                         when "0100" => DIGIT_CTRL :=
"0110011";
95.                                         when "0101" => DIGIT_CTRL :=
"1011011";
96.                                         when "0110" => DIGIT_CTRL :=
"1011111";
97.                                         when "0111" => DIGIT_CTRL :=
"1110000";
98.                                         when "1000" => DIGIT_CTRL :=
"1111111";
99.                                         when "1001" => DIGIT_CTRL :=
"1111011";
100.                                        when others => DIGIT_CTRL :=
"0000000";
101.                                     end case;
102.                                     else
103.                                         DIGIT_VAL := ONES_BUS;
104.                                         CUR_DIGIT := ONES;
105.                                         COMMONS_CTRL := "000";
106.                                     end if;
107.
108.                                     COMM_ONES      <= not COMMONS_CTRL(0);
109.                                     COMM_DECS      <= not COMMONS_CTRL(1);
110.                                     COMM_HUNDREDS <= not COMMONS_CTRL(2);
111.
112.                                     SEG_A <= not DIGIT_CTRL(6);
113.                                     SEG_B <= not DIGIT_CTRL(5);
114.                                     SEG_C <= not DIGIT_CTRL(4);
115.                                     SEG_D <= not DIGIT_CTRL(3);
116.                                     SEG_E <= not DIGIT_CTRL(2);
117.                                     SEG_F <= not DIGIT_CTRL(1);
118.                                     SEG_G <= not DIGIT_CTRL(0);
119.                                     DP      <= '1';
120.
121.                                     end if;
122.                                     end process INDICATE;
123.
124.                                     end Behavioral;

```

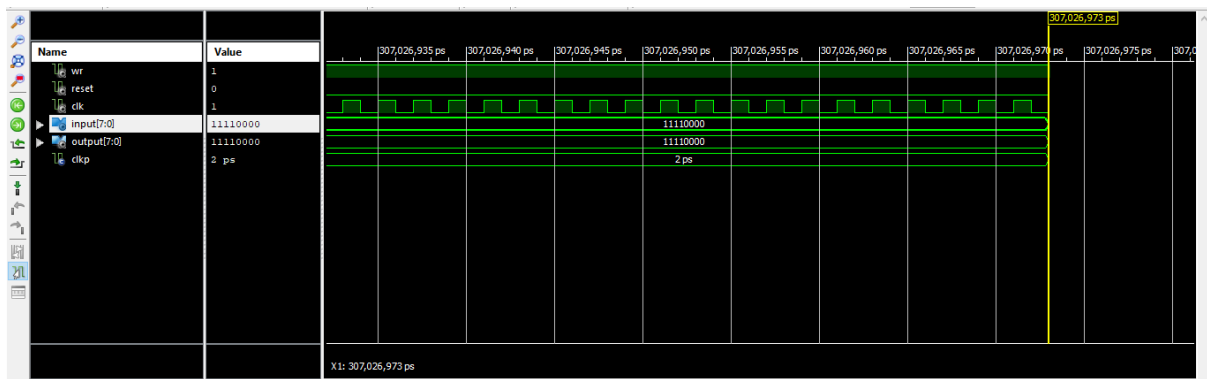


Рис. 2 – Часова діаграма ACC

 


Рис. 3 – Часова діаграма ALU

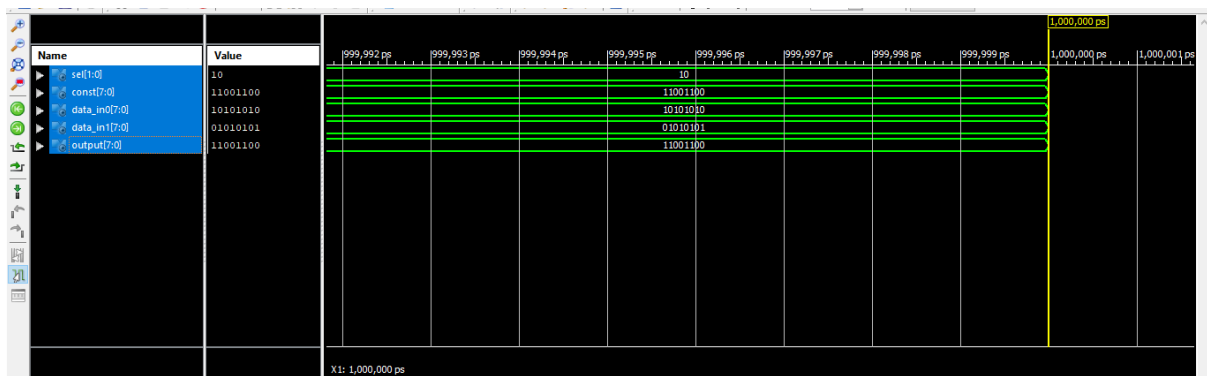


Рис. 4 – Часова діаграма MUX

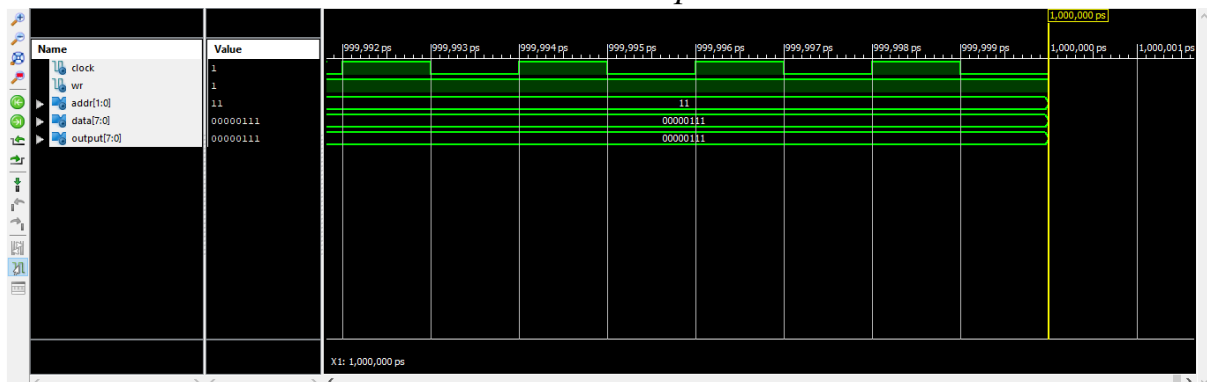


Рис. 5 – Часова діаграма RAM

 


Рис 6. – Часова діаграма SEG_DECODER

 


Рис 7. – Часова діаграма TopLevel

Файл TopLevelTest.vhd

```

1.  LIBRARY ieee;
2.  USE ieee.std_logic_1164.ALL;
3.  USE ieee.numeric_std.ALL;
4.  LIBRARY UNISIM;
5.  USE UNISIM.Vcomponents.ALL;
6.  ENTITY TopLevel_TopLevel_sch_tb IS
7.  END TopLevel_TopLevel_sch_tb;
8.  ARCHITECTURE behavioral OF TopLevel_TopLevel_sch_tb IS
9.
10.   COMPONENT TopLevel
11.   PORT( CLOCK :      IN      STD_LOGIC;
12.         RESET      :      IN      STD_LOGIC;
13.         ENTER_OP1   :      IN      STD_LOGIC;
14.         ENTER_OP2   :      IN      STD_LOGIC;
15.         CALCULATE    :      IN      STD_LOGIC;
16.         DATA_IN     :      IN      STD_LOGIC_VECTOR (7 DOWNTO 0);
17.         COMMON_0_OUT :      OUT     STD_LOGIC;
18.         COMMON_1_OUT :      OUT     STD_LOGIC;
19.         COMMON_2_OUT :      OUT     STD_LOGIC;
20.         TEST         :      OUT     STD_LOGIC_VECTOR(7 downto 0);
21.         A_OUT        :      OUT     STD_LOGIC;
22.         B_OUT        :      OUT     STD_LOGIC;
23.         C_OUT        :      OUT     STD_LOGIC;
24.         D_OUT        :      OUT     STD_LOGIC;
25.         E_OUT        :      OUT     STD_LOGIC;
26.         F_OUT        :      OUT     STD_LOGIC;
27.         G_OUT        :      OUT     STD_LOGIC;
28.         DP_OUT       :      OUT     STD_LOGIC;

```

```

29.          RAMOUT: OUT STD_LOGIC_VECTOR(7 downto 0);
30.          ALUOUT: OUT STD_LOGIC_VECTOR(7 downto 0);
31.          RAMA: OUT STD_LOGIC_VECTOR(1 downto 0);
32.          RAMWR: OUT STD_LOGIC;
33.          OVERFLOW :      OUT      STD_LOGIC);
34.      END COMPONENT;
35.
36.      SIGNAL CLOCK      :      STD_LOGIC := '0';
37.      SIGNAL RESET      :      STD_LOGIC;
38.      SIGNAL ENTER_OP1  :      STD_LOGIC;
39.      SIGNAL ENTER_OP2  :      STD_LOGIC;
40.      SIGNAL CALCULATE  :      STD_LOGIC;
41.      SIGNAL DATA_IN   :      STD_LOGIC_VECTOR (7 DOWNT0 0);
42.      SIGNAL COMMON_0_OUT :      STD_LOGIC;
43.      SIGNAL COMMON_1_OUT :      STD_LOGIC;
44.      SIGNAL COMMON_2_OUT :      STD_LOGIC;
45.      SIGNAL A_OUT      :      STD_LOGIC;
46.      SIGNAL B_OUT      :      STD_LOGIC;
47.      SIGNAL C_OUT      :      STD_LOGIC;
48.      SIGNAL D_OUT      :      STD_LOGIC;
49.      SIGNAL E_OUT      :      STD_LOGIC;
50.      SIGNAL F_OUT      :      STD_LOGIC;
51.      SIGNAL G_OUT      :      STD_LOGIC;
52.      SIGNAL DP_OUT     :      STD_LOGIC;
53.      SIGNAL OVERFLOW   :      STD_LOGIC;
54.      SIGNAL TEST: STD_LOGIC_VECTOR(7 downto 0);
55.      SIGNAL TEST2: STD_LOGIC_VECTOR(7 downto 0);
56.      signal RAMOUT: STD_LOGIC_VECTOR(7 downto 0);
57.      signal ALUOUT: STD_LOGIC_VECTOR(7 downto 0);
58.      signal RAMA: STD_LOGIC_VECTOR(1 downto 0);
59.      signal RAMWR: STD_LOGIC;
60.
61.  --      constant CLOCK_period : time := 166ns;
62.      constant CLKP: time := 12ms;--24ms;
63.
64.  BEGIN
65.
66.      UUT: TopLevel PORT MAP(
67.          CLOCK => CLOCK,
68.          RESET => RESET,
69.          ENTER_OP1 => ENTER_OP1,
70.          ENTER_OP2 => ENTER_OP2,
71.          CALCULATE => CALCULATE,
72.          DATA_IN => DATA_IN,
73.          COMMON_0_OUT => COMMON_0_OUT,
74.          COMMON_1_OUT => COMMON_1_OUT,
75.          COMMON_2_OUT => COMMON_2_OUT,
76.          A_OUT => A_OUT,
77.          B_OUT => B_OUT,
78.          C_OUT => C_OUT,
79.          D_OUT => D_OUT,
80.          E_OUT => E_OUT,
81.          F_OUT => F_OUT,
82.          G_OUT => G_OUT,
83.          DP_OUT => DP_OUT,
84.          OVERFLOW => OVERFLOW,
85.          TEST => TEST,
86.          RAMOUT => RAMOUT,
87.          ALUOUT => ALUOUT,
88.          RAMA => RAMA,
89.          RAMWR => RAMWR
90.      );
91.
92.      CLOCK_process: process
93.      begin
94.          CLOCK <= '0';

```

```

95.          wait for 83ns;
96.          CLOCK <= '1';
97.          wait for 83ns;
98.    end process;
99.
100.    -- *** Test Bench - User Defined Section ***
101.    tb : PROCESS
102.    BEGIN
103.        lp1: for i in 2 to 2 loop
104.            lp2: for j in 4 to 4 loop
105.                TEST2 <= std_logic_vector((to_signed(j - i, 8) sll
1) + i + 10));
106.                ENTER_OP1 <= '1';
107.                ENTER_OP2 <= '1';
108.                CALCULATE <= '1';
109.                DATA_IN <= (others => '0');
110.                RESET <= '0';
111.                wait for CLKP;
112.                RESET <= '1';
113.                wait for CLKP;
114.                DATA_IN <= std_logic_vector(to_unsigned(i, 8)); -- A
115.                ENTER_OP1 <= '0';
116.                wait for CLKP;
117.                ENTER_OP1 <= '1';
118.                wait for CLKP;
119.                DATA_IN <= std_logic_vector(to_unsigned(j, 8)); -- B
120.                ENTER_OP2 <= '0';
121.                wait for CLKP;
122.                ENTER_OP2 <= '1';
123.                wait for CLKP;
124.                CALCULATE <= '0'; -- START CALCULATION
125.                wait for CLKP* 7;
126.                assert TEST = TEST2 severity FAILURE;
127.                wait for CLKP;
128.            end loop;
129.        end loop;
130.
131.        WAIT; -- will wait forever
132.    END PROCESS;
133.    -- *** End Test Bench - User Defined Section ***
134.
135.    END;

```

 


Рис.8 – 7-сегментний індикатор

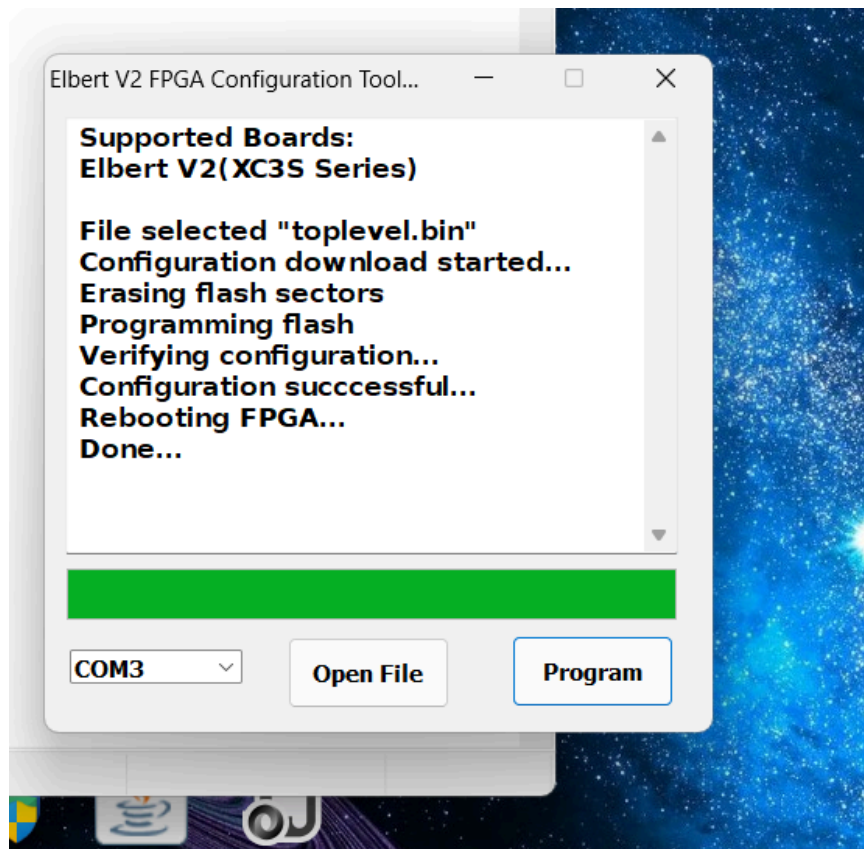


Рис.9 – Успішна прошивка

Висновок: Виконуючи дану лабораторну роботу я навчився реалізовувати цифровий автомат для обчислення значення виразів використовуючи засоби VHDL.